

# Electricity

## Key Vocabulary

<b>circuit</b>	A path that an electrical <b>current</b> can flow around.
<b>symbol</b>	A visual picture that stands for something else.
<b>cell/battery</b>	A device that stores chemical energy until it is needed. A <b>cell</b> is a single unit. A <b>battery</b> is a collection of <b>cells</b> .
<b>current</b>	The flow of <b>electrons</b> , measured in <b>amps</b> .
<b>amps</b>	How electric <b>current</b> is measured.
<b>voltage</b>	The force that makes the electric <b>current</b> move through the wires. The greater the <b>voltage</b> , the more <b>current</b> will flow.
<b>resistance</b>	The difficulty that the electric <b>current</b> has when flowing around a <b>circuit</b> .
<b>electrons</b>	Very small particles that travel around an electrical <b>circuit</b> .

## Key Knowledge

A series circuit is a circuit that has only one route for the current to take. If more bulbs or buzzers are added, the power has to be shared and so they will be dimmer or quieter.

If just one part of a series circuit breaks, the circuit is broken and the flow of current stops. For example disconnecting a wire or opening a switch.

### Brighter and Louder:

More batteries or a higher voltage will make components brighter or louder. Shortening the wires means the electrons have less resistance to flow through.

### Dimmer and Quieter:

Less batteries or a lower voltage will make components duller or quieter. Lengthening the wires means the electrons have to travel through more resistance.

