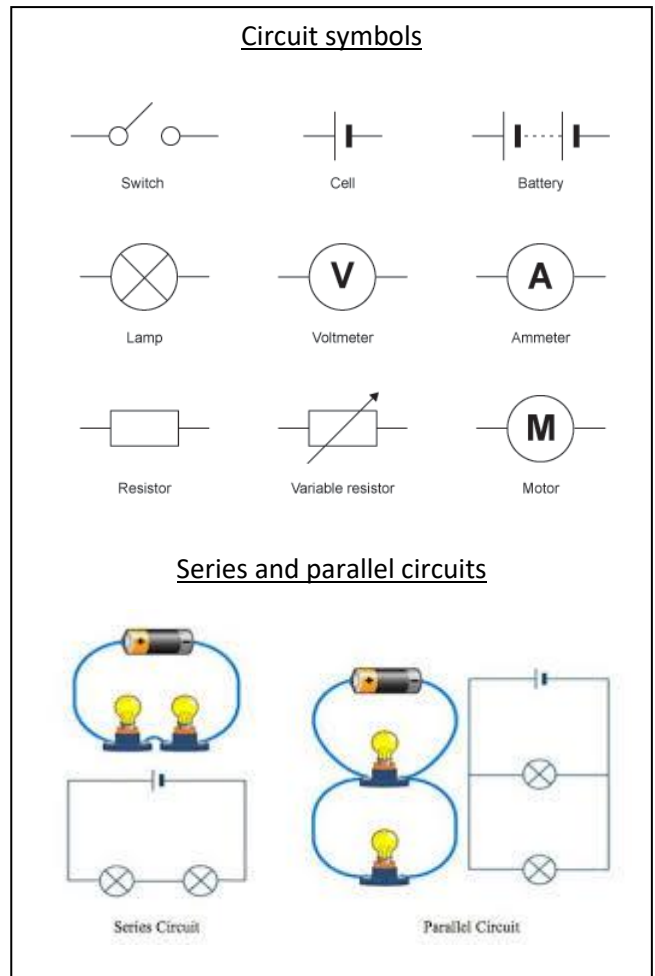


## Electricity – knowledge organiser

Key knowledge	
What is electricity?	<ul style="list-style-type: none"> <li>Electricity is created by <b>generators</b> which can be powered by gas, coal, oil, wind or solar.</li> <li>Electricity is the presence or flow of <b>charged particles</b>.</li> <li>An electric current is the flow of <b>electrons</b> around a circuit.</li> <li>The electrical energy can be converted into other types of energy such as light, heat, movement or sound.</li> <li>Electricity is <b>dangerous</b>, so be careful when using electrical appliances.</li> </ul>
What uses electricity?	<ul style="list-style-type: none"> <li>Lots of things use electricity including:                             <ul style="list-style-type: none"> <li>TV</li> <li>Hair dryer</li> <li>Cooker</li> <li>Lights</li> <li>Games consoles</li> </ul> </li> </ul>
Mains or Battery?	<ul style="list-style-type: none"> <li>Appliances that use electricity get it either from the mains (need to be plugged in) such as a TV or washing machine</li> <li>Some get their electricity from a battery such as a torch</li> <li>Some might need to be plugged in to charge a battery like a mobile phone</li> </ul>
Electrical circuits	Electricity can flow through the components in a complete electric circuit. A circuit always needs a power source, such as a battery. A circuit can also contain other electrical components, such as bulbs, buzzers or motors.
Switches	When a switch is open (off), there is a gap in the circuit. Electricity cannot travel around the circuit. When a switch is closed (on), it makes the circuit complete. Electricity can travel around the circuit.
Changing circuits	<p>More batteries</p> <ul style="list-style-type: none"> <li>Adding more batteries to a simple circuit will increase the electrical energy, which will make a bulb brighter.</li> </ul> <p>More bulbs</p> <ul style="list-style-type: none"> <li>Adding more bulbs to a simple circuit will reduce the electrical energy and make the bulbs dimmer.</li> </ul> <p>Longer wires</p> <ul style="list-style-type: none"> <li>Lengthening the wires in a simple circuit will reduce the electrical energy, as it has further to travel. The extra distance will make the bulb dimmer.</li> </ul>
Scientists we need to know about	
5 facts about Michael Faraday	<ul style="list-style-type: none"> <li>Michael Faraday was born on September 22, 1791</li> <li>His father was a blacksmith</li> <li>Due to money constraints, Faraday had to leave school at the age of 13</li> <li>In 1821, he proved that magnetism that was created by an electric current could set a magnet in motion.</li> <li>He made the very first dynamo which was used in electricity generation. It was this discovery that opened the path to the age of electricity.</li> </ul>



### Key Vocabulary

**Ammeter** - A device used to measure electric current.

**Ampere** - Unit of current, eg the current in the bulb is 4 amps or amperes (A).

**Battery** - A chemical supply of electrical energy. For example, common battery voltages include 1.5 V and 9 V.

**Cell** - A store of internal energy that can be transferred as an electric current in a circuit.

**Circuit** - A closed loop through which current moves - from a power source, through a series of components, and back into the power source.

**Circuit diagram** - A diagram that represents an electric circuit using lines and symbols.

**Circuit symbol** - Diagram used to represent an electrical component in a circuit diagram.

**Conductor** - A material which allows charge to move easily through it.

**Electric current** - The movement of electrically charged particles, for example, electrons moving through a wire or ions moving through a solution.

**Electron** - Subatomic particle, with a negative charge and a negligible mass relative to protons and neutrons.

**Insulator** - Material that does not allow charge or heat to pass through it easily.

**Ohms** - The unit of electrical resistance, whose symbol is  $\Omega$ .

**Parallel** - In a parallel circuit, the current divides into two or more paths before recombining to complete the circuit

**Potential difference (voltage)** - A measure of the energy given to the charge carriers in a circuit.

**Resistance** - The opposition in an electrical component to the movement of electrical charge through it. Resistance is measured in ohms.

**Series** - Connected to a circuit in such a way that the same current flows through each component in turn. Opposite of in parallel.

**Volt** - Unit of voltage. For example, the voltage across the lamp was 6 volts (V).

**Voltmeter** - A device used to measure potential difference or voltage.