

Sholing Junior School - Science

Topic: Electricity

Year: 4

Strand: Physics

What should I already know?

- **Electricity** is a form of **energy** that can be carried by wires and is used for heating and lighting, and to provide **power** for **devices**.
- **Sources** of light and sound may need **electricity** to work.

What I will learn

I will:

- Identify common appliances that run on electricity
- Construct a simple series electrical circuit, identifying and naming its basic parts, including cells, wires, bulbs, switches and buzzers
- Identify whether or not a lamp will light in a simple series circuit, based on whether or not the lamp is part of a complete loop with a battery
- Recognise that a switch opens and closes a circuit and associate this with whether or not a lamp lights in a simple series circuit
- Recognise some common conductors and insulators, and associate metals with being good conductors.

Investigate!

We will construct simple series circuits, trying different components, for example, bulbs, buzzers and motors, and including switches, and use my circuits to create simple devices.

We will draw the circuit as a pictorial representation.

We might use the terms current and voltage and we will be taught about precautions for working safely with electricity.

We will work scientifically by: observing patterns, for example, that bulbs get brighter if more cells are added, that metals tend to be conductors of electricity, and that some materials can and some cannot be used to connect across a gap in a circuit.


How does a circuit work?

- A complete circuit is a loop that allows **electrical current** to flow through **wires**.
- A circuit contains a **battery (cell)**, **wires** and an **appliance** that requires **electricity** to work (such as a **bulb**, **motor** or **buzzer**).
- The **electrical current** flows through the wires from the **battery (cell)** to the **bulb**, **motor** or **buzzer**.
- A **switch** can break or reconnect a circuit.
- A **switch** controls the flow of the **electrical current** around the circuit. When the **switch** is off, the **current** cannot flow. This is not the same as an incomplete circuit.

What are electrical conductors and insulators?

- When objects are placed in the circuits, they may or may not allow **electricity** to pass through.
- Objects that are made from materials that allow **electricity** to pass through a create a complete circuit are called **electrical conductors**.
- Objects that are made from materials that do not allow **electricity** to pass through and do not complete a circuit are called **electrical insulators**.

Vocabulary

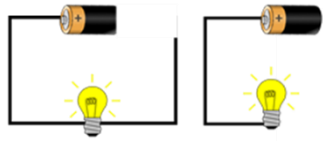appliances	A device or machine in your home that you use to do a job such as cleaning or cooking. Appliances are often electrical .
battery	Small devices that provide the power for electrical items such as torches
bulb	The glass part of an electric lamp , which gives out light when electricity passes through it.
buzzer	An electrical device that is used to make a buzzing sound
cell	A synonym for battery
circuit	A complete route which an electric current can flow around. These are incomplete examples. 
component	The parts that something is made of
conductor	A substance that heat or electricity can pass through or along
current	A flow of electricity through a wire or circuit
device	An object that has been invented for a particular purpose
electricity	A form of energy that can be carried by wires and is used for heating and lighting, and to provide power for devices
energy	The power from sources such as electricity that makes machines work or provides heat
fuel	A substance such as coal, oil, or petrol that is burned to provide heat or power
generate	Cause it to begin and develop
insulator	A non- conductor of electricity or heat
mains	Where the supply of water, electricity , or gas enters a building
motor	A device that uses electricity or fuel to produce movement
power	Power is energy , especially electricity , that is obtained in large quantities from a fuel source and used to operate lights, heating, and machinery.
source	Where something comes from
switch	A small control for an electrical device which you use to turn the device on or off
wires	A long thin piece of metal that is used to fasten things or to carry electric current

Electrical Safety Tips For your Home What You Should Know

