




As a Scientist...

Key Vocabulary	
circuit	A path that an electrical current can flow around.
symbol	A visual picture that stands for something else.
cell/battery	A device that stores chemical energy until it is needed. A cell is a single unit. A battery is a collection of cells .
current	The flow of electrons , measured in amps .
amps	How electric current is measured.
voltage	The force that makes the electric current move through the wires. The greater the voltage , the more current will flow.
resistance	The difficulty that the electric current has when flowing around a circuit .
electrons	Very small particles that travel around an electrical circuit .

Key Knowledge

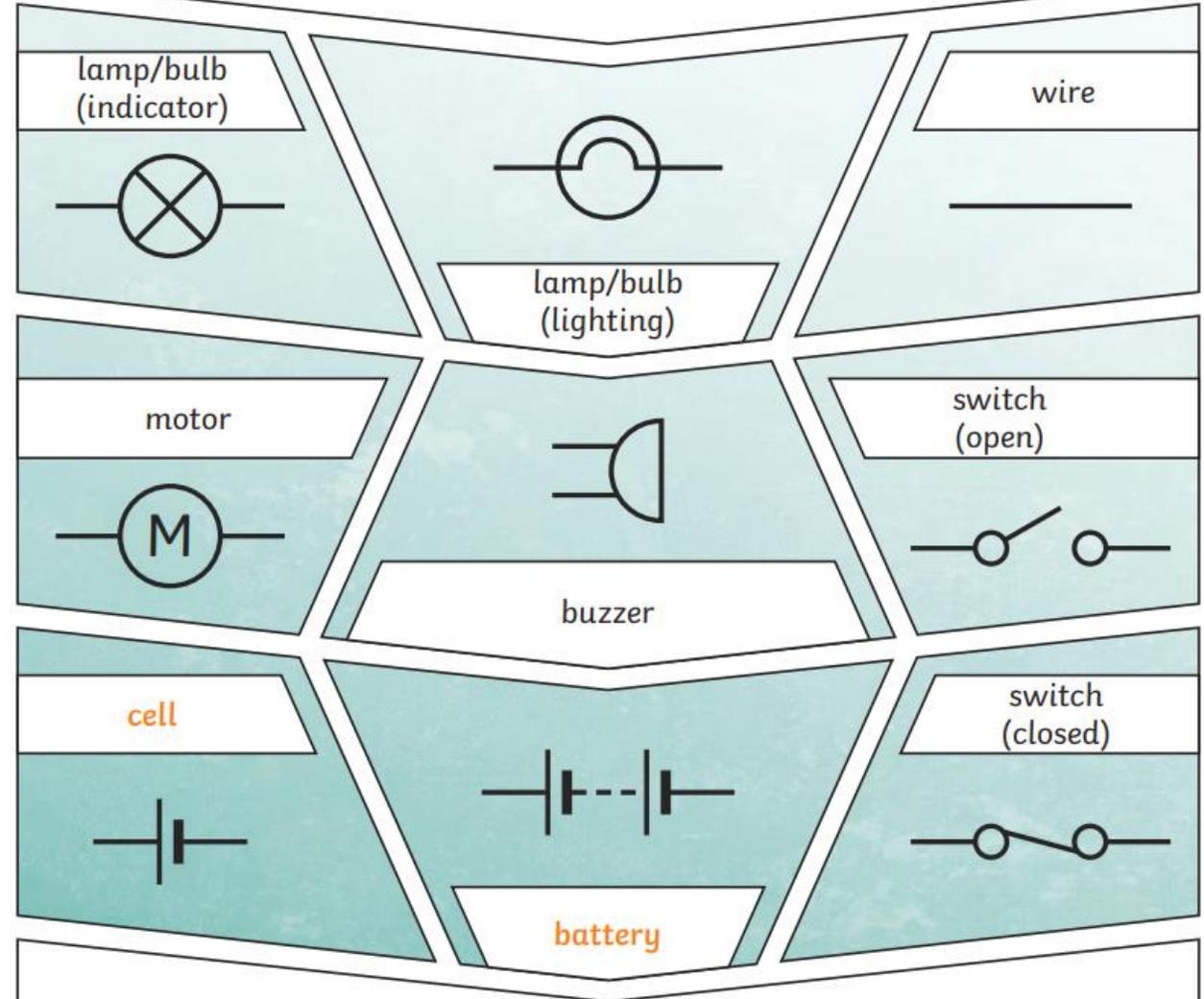Components of a **Circuit** and Their **Symbols**



These **symbols** can be used to create electrical **circuit** diagrams.




As a Scientist...

Key Knowledge

What will make a bulb brighter or a buzzer louder?

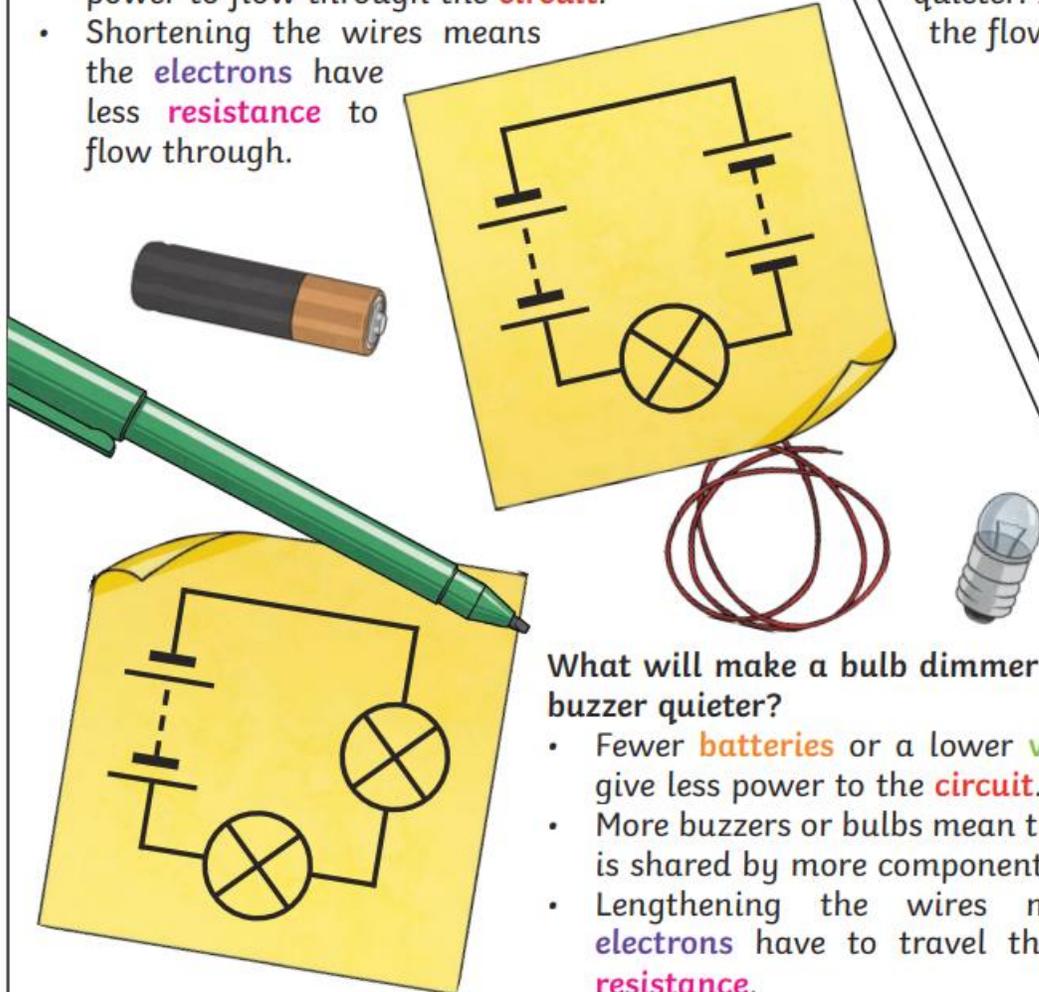- More **batteries** or a higher **voltage** create more power to flow through the **circuit**.
- Shortening the wires means the **electrons** have less **resistance** to flow through.




Series Circuit

A **circuit** that has only one route for the **current** to take. If more bulbs or buzzers are added, the power has to be shared and so they will be dimmer or quieter. If just one part of this series **circuit** breaks, the **circuit** is broken and the flow of **current** stops.

What will make a bulb dimmer or a buzzer quieter?

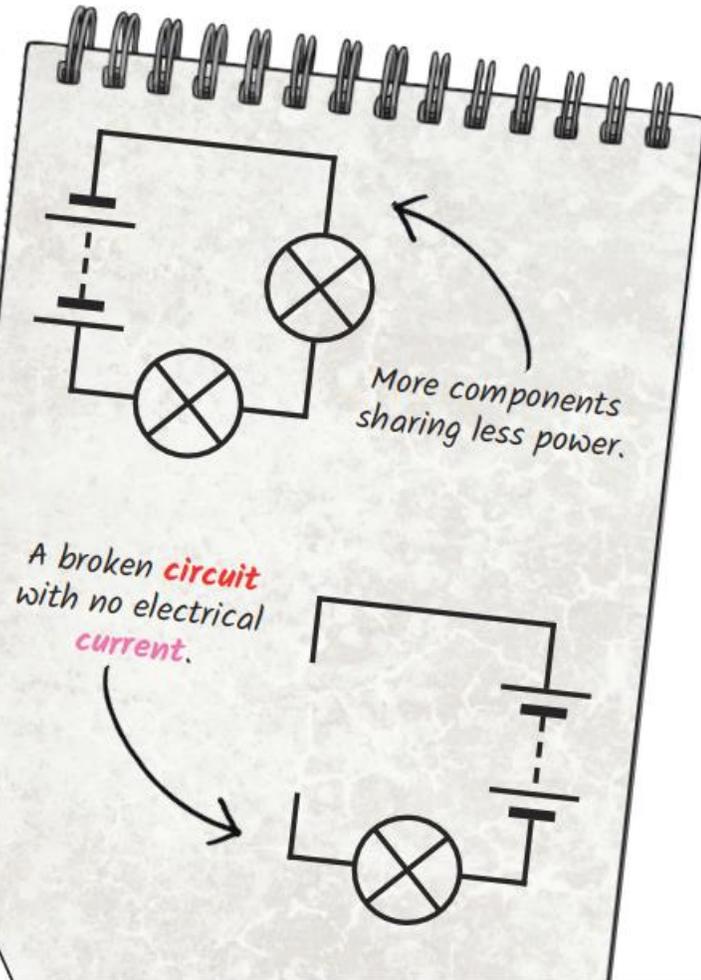- Fewer **batteries** or a lower **voltage** give less power to the **circuit**.
- More buzzers or bulbs mean the power is shared by more components.
- Lengthening the wires means the **electrons** have to travel through more **resistance**.





As a Scientist...

In Year 4 I learnt to:

- Identify common appliances that run on electricity.
- Construct a simple series electrical circuit, identifying and naming its basic parts, including cells, wires, bulbs, switches and buzzers.
- Identify whether or not a lamp will light in a simple series circuit, based on whether or not the lamp is part of a complete loop with a battery.
- Recognise that a switch opens and closes the circuit and associate this with whether or not a lamp lights in a simple series circuit.
- Recognise some common conductors and insulators, and associate metals with being good conductors.
- Know the difference between a conductor and an insulator; giving examples of each.
- Safety when using electricity.

In year 6: I will learn to:

- Associate the brightness of a lamp or the volume of a buzzer with the number and voltage of cells used in the circuit.
- Compare and give reasons for variations in how components function, including the brightness of bulbs, the loudness of buzzers and the on/off position of switches.
- Use recognised symbols when representing a simple circuit in a diagram.