 L \	1
NAME:	1
1	-
1	
1	
1	



Exit Pass
8.1.1 Memory
☐ I can name the two types of memory in a computer system.
See County
☐ I can define the term memory.
APDCOSITOP
APDCOSITOP
☐ I can describe the differences between RAM & ROM.
Difference 1
Difference 1
Difference 2

 ! NAME:	
I HAME.	computer science
1	Exit Pass
1 '	

l 1 _	
	8.1.2 Storage
00	☐ I can name the three categories of secondary storage.
	1 e.g
	2 e.g
	3e.g
00	☐ I can define the term secondary storage.
	N-VHWDISWNIU
_	
_	
00	I can identify the differences and similarities between memory and storage

	RAM	Secondary Storage
Volatile		
Editable		
Holds data that is open/in use		
Holds data that is not in use		
Non-volatile		
Can be accessed by the CPU		
High capacity		

NAME:	 _		1
1 1 1			



8.1.3 Secondary Storage



☐ I can state the 6 characteristics of secondary storage















- I can describe the HDD using each characteristic. Cost – How much money a device is to buy. 1. 2.

I can choose the most suitable storage device for given scenarios.

Apu has a handheld e-book	reader that allows h	nim to store and read	d electronic books



Types of secondary storage devices are magnetic, optical or solid state.


State which type of storage is most suitable for storing the electronic books inside the e-book reader.

(ii) Explain one reason why this type of storage is the most suitable.

 NAME:	- 	Co
1		



8.2.1 Binary to Denary

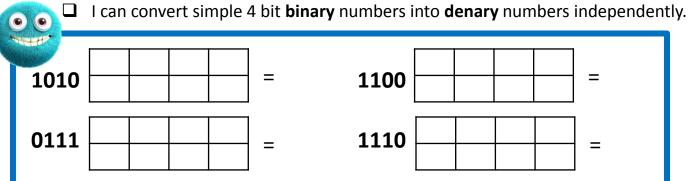

☐ I can con	vert bi	nary r	numbe	ers to c	lenary	, numl	bers.	
1011 1001								=
0111 1011								=

|--|

1 0011 0110

1 1001 1001 = =

 NAME: 		@ [MP	U Exi		80		
○ □ 1c	an convert s	imple denar			nary t			ependentl
13 7				2 [11 [
<u> </u>	l can conv	ert denary	numbe	ers to b	inary n	umbers	5.	
75								
138								
	an convert	denary (2	55+) ทเ	umbers	to bina	ary nun	nbers.	
300	256							
407	256							

NAME:


8.2.5 Binary Addition


00		I explain WHY 1+1 is 10 and 1+ 1+ 1 = 11 in binary.
----	--	---


1 + 1 in binary = 10 because______

1+1+1 in binary is 11 because _____



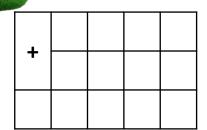

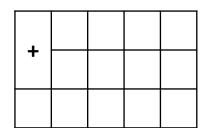

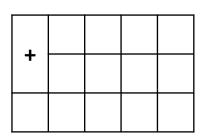


I can add 8 bit binary numbers together and explain what an overflow error is.

An overflow error occurs when...

	1	0	1	1	0	1	1	0
•	1	1	1	1	1	1	0	1

•	0	1	1	0	0	1	0	1
_	0	1	0	1	0	1	1	0

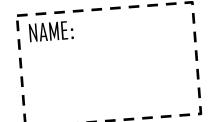




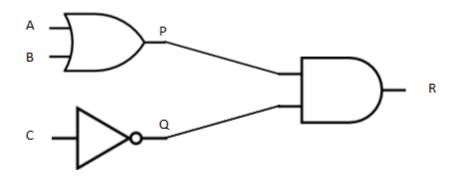8.2.6 Logic Gates

1 Identify the following logic gates.



Fill in the appropriate values in the truth table shown below for the following logic gate diagram.



Α	В	С	P	Q	R
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			